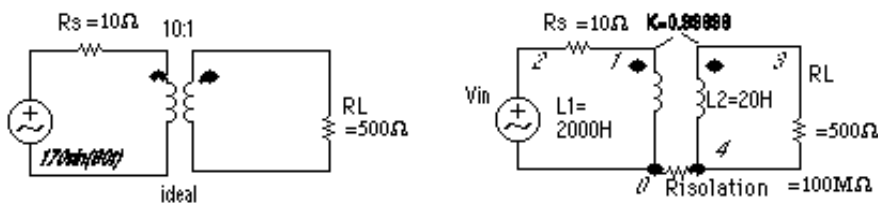


SPICE simulation of an ideal transformers


An ideal transformer can be simulated using mutually coupled inductors. An ideal transformer has a coupling coefficient $k=1$ and very large inductances. However, Spice does not allow a coupling coefficient of $k=1$. The ideal transformer can be simulated in Spice by making k close to one, and the inductors $L1$ and $L2$ very large, such that $\omega L1$ and $\omega L2$ is much larger than the resistors in series with the inductors. The secondary circuit needs a DC connection to ground. This can be accomplished by adding a large resistor to ground or giving the primary and secondary circuits a common node.

The following example illustrates how to simulate a transformer.



For the above example, let's make $\omega L2 \gg 500 \text{ Ohm}$ or $L2 > 500/(60 \cdot 2\pi)$; let's make $L2$ at least 10 times larger, ex. $L2=20\text{H}$. $L1$ can then be found from the turn ratio: $L1/L2 = (N1/N2)^2$. For a turn ratio of 10 this makes $L1=L2 \times 100=2000\text{H}$. We make K close to 1 let's say 0.99999.

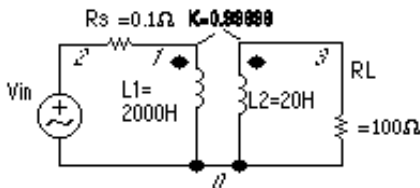A Spice input listing is given below for the following circuit.



Example transformer

```
VIN 2 0 SIN(0 170 60 0 0)
```

```
* This defines a sinusoid of 170 V amplitude and 60 Hz. RS 2 1 10
```

```
L1 1 0 2000
```

```
L2 3 0 20
```

```
K L1 L2 0.99999
```

```
RL 3 0 500
```

```
.TRAN 0.2M 25M
```

```
.PLOT TRAN V(2)
```

```
.PLOT TRAN V(3)
```

```
.END
```

[Back to Spice Guidelines](#)

Jan Van der Spiegel;

jan@ee.upenn.edu

Created Sept. 30, 1995; Updated Aug. 1, 1995